

Pass Transistors and Transmission Gates

The strength of a signal is measured by how closely it approximates an ideal voltage source.

In general, the stronger a signal, the more current it can source or sink.

An nMOS transistor is an almost perfect switch when passing a 0 and thus we say it passes a strong 0. However, the nMOS transistor is imperfect at passing a 1. The high voltage level is somewhat less than VDD.

A pMOS transistor again has the opposite behavior, passing strong 1s but degraded 0s. When an nMOS or pMOS is used alone as an imperfect switch, we sometimes call it a pass transistor.

 


FIGURE 1.20 Pass transistor strong and degraded outputs

By combining an nMOS and a pMOS transistor in parallel (Figure 1.21(a)), we obtain a switch that turns on when a 1 is applied to g (Figure 1.21(b)) in which 0s and 1s are both passed in an acceptable fashion (Figure 1.21(c)). We term this a transmission gate or pass gate.


 


FIGURE 1.21 Transmission gate


Some logic design using Transmission Gates

- 2:1 Multiplexer

 

When $S=0$, $\bar{S} = 1$, then, PMOS and NMOS of B will be ON and $Z = A.0 + B.1 = B$

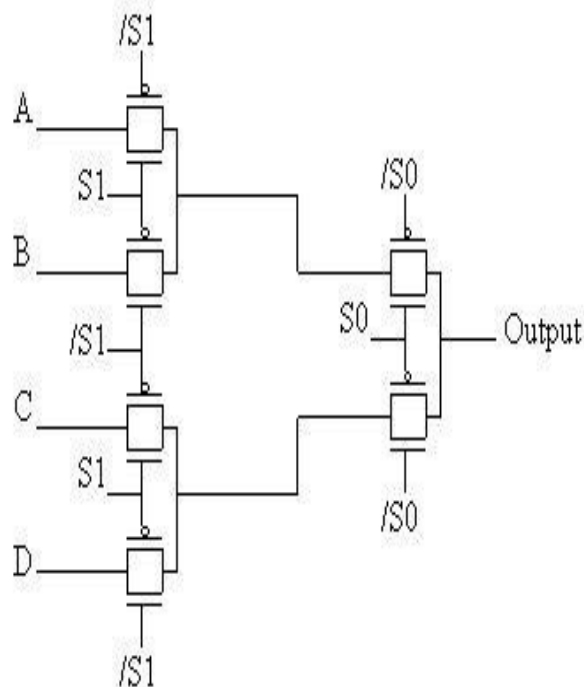When $S=1$, $\bar{S} = 0$, then, PMOS and NMOS of A will be ON and $Z = A.1 + B.0 = A$



When $S1=0$, $\bar{S1}=1$,
B and D turns ON, and,
When $S0=0$, $\bar{S0}=1$,
D is selected and
appears at the output.

When $S1=0$, $\bar{S1}=1$,
B and D turns ON, and,
When $S0=1$, $\bar{S0}=0$,
B is selected and
appears at the output.

When $S1=1$, $\bar{S1}=0$,
A and C turns ON, and,
When $S0=0$, $\bar{S0}=1$,
C is selected and
appears at the output.

When $S1=1$, $\bar{S1}=0$,
A and C turns ON, and,
When $S0=1$, $\bar{S0}=0$,
A is selected and
appears at the output.

Latches

A D-latch built from a 2-input multiplexer and two inverters is shown in Figure 1.31(a). The multiplexer can be built from a pair of transmission gates, shown in Figure 1.31(b), because the inverters are restoring. This latch also produces a complementary output, \bar{Q} . When $\text{CLK} = 1$, the latch is transparent and D flows through to Q (Figure 1.31(c)). When CLK falls to 0, the latch becomes opaque. A feedback path around the inverter pair is established (Figure 1.31(d)) to hold the current state of Q indefinitely. The D latch is also known as a level-sensitive latch because the state of the output is dependent on the level of the clock signal, as shown in Figure 1.31(e). The latch shown is a positive-level-sensitive latch, represented by the symbol in Figure 1.31(f). By inverting the control connections to the multiplexer, the latch becomes negative-level-sensitive.

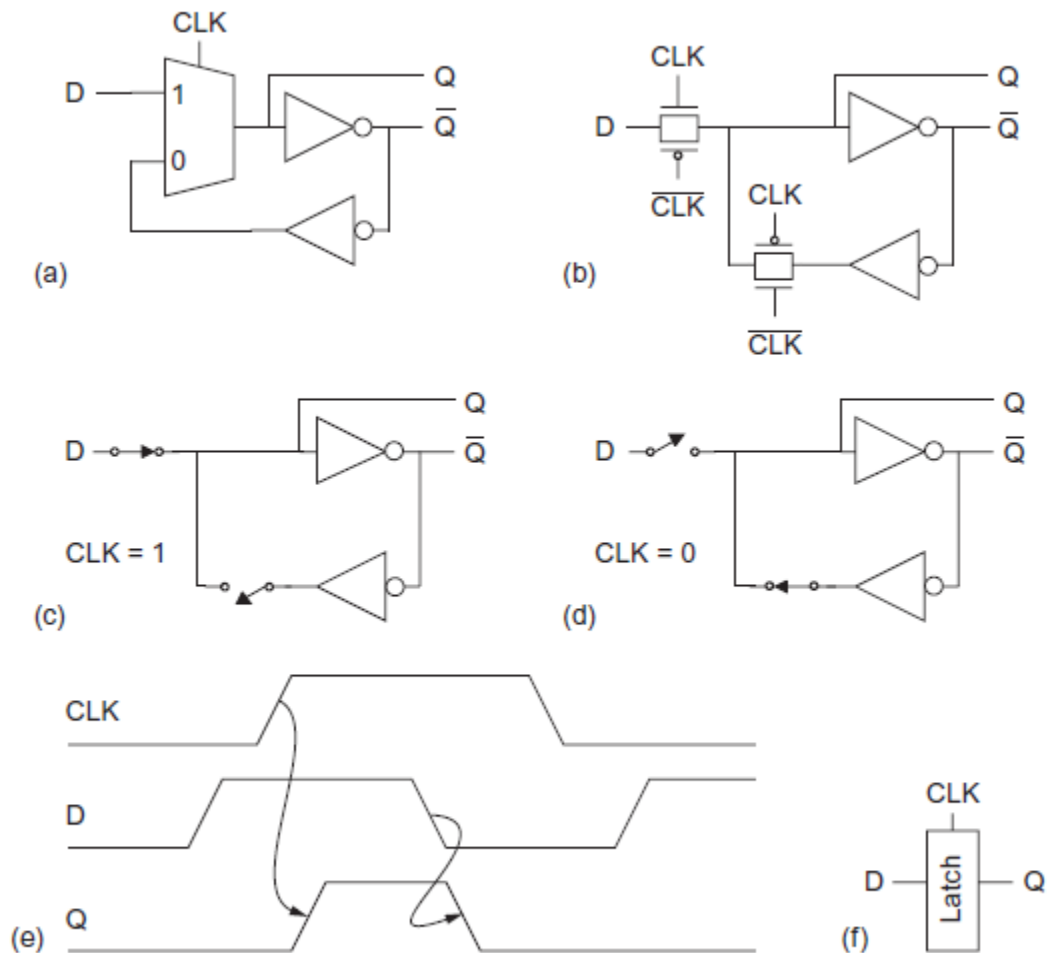


FIGURE 1.31 CMOS positive-level-sensitive D latch